

Electric Current

Textbook pages 280–289

Before You Read

What is needed for a light bulb to light up? Write your ideas on the lines below.

Mark the Text

Check for Understanding

As you read this section, be sure to reread any parts you do not understand. Highlight any sentences that help you develop your understanding.

Reading Check

1. What is an electric circuit?

Reading Check

2. What is the name of the device used to measure electric current?

What is needed for charges to move through an electric circuit?

A continuous movement of charge through a conductor is called **current electricity**. A complete pathway through which electrons can flow is called an **electric circuit**. An electric circuit has the following basic parts:

- ◆ There must be a *source* of electrical energy. This may be a battery or a wall outlet.
- ◆ There must be a *conductor* through which charges can move. This is usually a metal wire.
- ◆ There must be a device, called a *load*, which converts electrical energy into other forms of energy such as light or sound. Light bulbs, speakers, heaters, and motors are examples of loads.
- ◆ There may be a *switch*—a device that can control the movement of charges in the circuit by turning it on (closing the circuit) or turning it off (opening the circuit). ✓

What is electric current and how is it measured?









An electrical source such as a battery provides energy to push negative charges through the conducting wires in a circuit. This movement of charge is called *current*. **Electric current** is the amount of charge that passes a point in a conducting wire each second.


Electric current is measured in units called **amperes (A)**. A current of one ampere (1.0 A) is produced when 1.0 C (coulombs) of charged particles move past a point in a circuit each second. Electric current is measured with a device called an **ammeter**. ✓

What does an electric circuit look like?

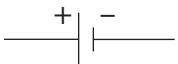The parts of a circuit can be drawn with symbols to show how the circuit is connected. A picture that is made using these symbols to represent an actual circuit is called a **circuit diagram**.

Examples of symbols used in circuit diagrams:

	conducting wire		bulb
	cell		open switch
	battery		closed switch
	voltmeter		ammeter

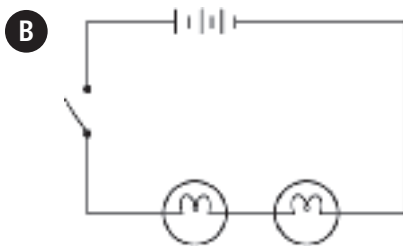

This circuit diagram (B) shows the parts of the circuit (A). Find each of the objects from circuit A in circuit B.








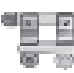

Name _____

Date _____


Use with textbook pages 280–285.

Identifying circuit symbols

Match the Term in the first column with the correct Illustration and Circuit Symbol in the other two columns. Place the corresponding letter and Roman numeral in the blank spaces provided.

Term	Illustration	Circuit Symbol
1. bulb _____ _____	A. 	I. 
2. battery _____ _____	B. 	II. 
3. open switch _____ _____	C. 	III. _____
4. closed switch _____ _____	D. 	IV. 
5. conducting wire _____ _____	E. 	V. 

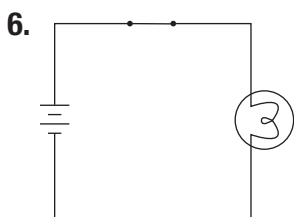
List all the parts in the following electrical circuit.



Use with textbook pages 280–285.

Drawing circuit diagrams

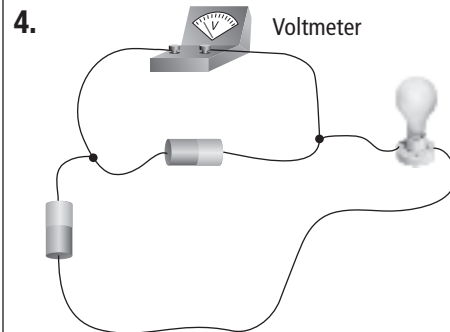Use circuit symbols to draw circuit diagrams for each of the following.



Use with textbook pages 280–285.

True or false?

Read the statements given below. If the statement is true, write “T” on the line in front of the statement. If it is false, write “F” and rewrite the statement to make it true.

1. _____ An electric circuit is a complete pathway through which electrons can flow.

2. _____ An electric load transforms light energy into electrical energy.

3. _____ Light bulbs, heaters, and batteries are all examples of electric loads.

4. _____ The wire through which electric current flows is a conductor.

5. _____ A switch is the source of electric potential energy in a circuit.

6. _____ Circuit diagrams use circuit symbols to illustrate actual electrical circuits.

7. _____ Current electricity is charge that remains stationary on an insulator.

8. _____ Electric current is the amount of charge passing a point in a conducting wire each second.

9. _____ Electric current is measured in volts.

10. _____ An ammeter is used to measure the current in a circuit.

Use with textbook pages 280–285.

Electric current

Match each Term on the left with the letter on the Diagram on the right. Each letter on the Diagram may be used only once.

Term	Diagram
1. _____ cell	
2. _____ bulb	
3. _____ switch	
4. _____ circuit diagram	
5. _____ conducting wire	

Circle the letter of the best answer.

6. What does the symbol represent?

- A. a load
- B. a battery
- C. a voltmeter
- D. an ammeter

7. Which of the following are correctly defined?


I.	ampere: unit for electric current
II.	ammeter: device used to measure current
III.	electric circuit: an incomplete pathway through which electrons can flow

- A. I and II only
- B. I and III only
- C. II and III only
- D. I, II, and III

8. Which of the following is not an example of an electric load?

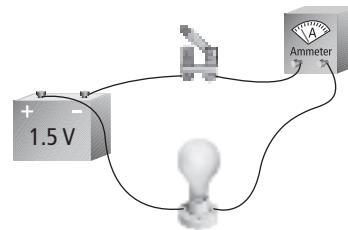- A. a motor
- B. a heater
- C. a light bulb
- D. a generator

Use the following diagram to answer question 9.



9. Which circuit diagram represents the illustration shown above?

