

Ohm's law – Try this! Voltage and Current in a Resistor (p315)

Resistor # 1

# of Cells	Voltage (V)	Current (mA)	Current (A)	$\frac{\text{voltage}}{\text{current}}$

Change in Voltage (RISE)	Change in Current (RUN)	Slope of the line ($\frac{\text{rise}}{\text{run}}$)

Resistor # 2

# of Cells	Voltage (V)	Current (mA)	Current (A)	$\frac{\text{voltage}}{\text{current}}$

Change in Voltage (RISE)	Change in Current (RUN)	Slope of the line ($\frac{\text{rise}}{\text{run}}$)